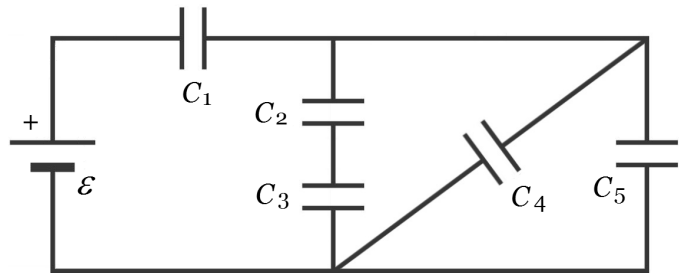


Example

In the circuit shown, $C_1 = C_4 = C_5 = C$ and $C_2 = C_3 = 2C$.


- a) Find the equivalent capacitance of the circuit.
- b) Find the energy stored in capacitor C_4 . Express your answers in terms of C and \mathcal{E} .



Problem

In the circuit shown, which is subtly different from the circuit in the example, $C_1 = C_4 = C_5 = C$ and $C_2 = C_3 = 2C$.

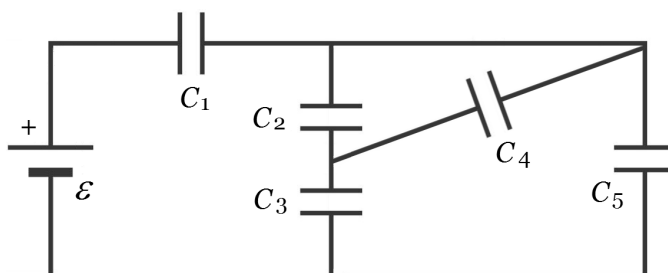
- a) Find the equivalent capacitance of the circuit.
- b) Find the energy stored in capacitor C_4 . Express your answers in terms of C and \mathcal{E} .



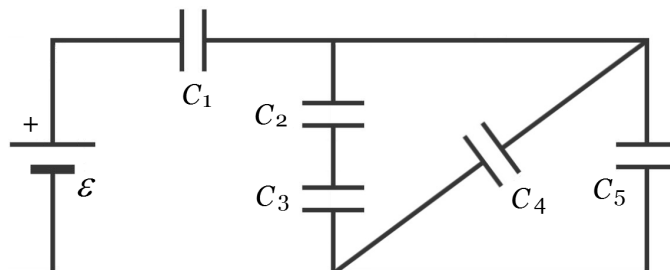Example

In the circuit shown, $C_1 = C_4 = C_5 = C$ and $C_2 = C_3 = 2C$.

- Find the equivalent capacitance of the circuit.
- Find the energy stored in capacitor C_4 . Express your answers in terms of C and \mathcal{E} .



- In order to find the equivalent capacitance of this circuit, one must first realize that capacitor C_4 is in parallel with C_5 and the branch containing capacitors C_2 and C_3 . This is true because the upper plates of C_2 , C_4 , and C_5 are connected by ideal wire and are thus at the same potential. The same is true of the bottom plates of C_3 , C_4 , and C_5 . Given this fact, one can begin reducing the circuit, starting with the two series capacitors C_2 and C_3 .

$$C_{23} = \left[\frac{1}{C_2} + \frac{1}{C_3} \right]^{-1} = \left[\frac{1}{2C} + \frac{1}{2C} \right]^{-1} = C$$

Next are the parallel capacitors C_{23} , C_4 , and C_5 .

$$C_{2345} = C_{23} + C_4 + C_5 = C + C + C = 3C$$

And finally the series capacitors C_1 and C_{2345} .

$$C_{\text{eq}} = \left[\frac{1}{C_1} + \frac{1}{C_{2345}} \right]^{-1} = \left[\frac{1}{C} + \frac{1}{3C} \right]^{-1} = \frac{3}{4}C$$

b) In order to find the energy stored in capacitor C_4 it is necessary to find the potential difference ΔV_4 across it. However, because C_{23} , C_4 , and C_5 are in parallel, the potential difference across each must be equal to the potential difference V_{2345} across their equivalent capacitor C_{2345} . Furthermore, since C_1 and C_{2345} are in series, they must hold the same charge, which is the same as the charge on the equivalent capacitor. Thus:

$$\Delta V_4 = \Delta V_{2345} = \frac{Q_{\text{eq}}}{C_{2345}} = \frac{3C\mathcal{E}/4}{3C} = \mathcal{E}/4$$


So the energy stored in capacitor C_4 is:

$$U_4 = \frac{1}{2}C_4(\Delta V_4)^2 = \frac{1}{2}C(\mathcal{E}/4)^2 = \frac{C\mathcal{E}^2}{32}$$

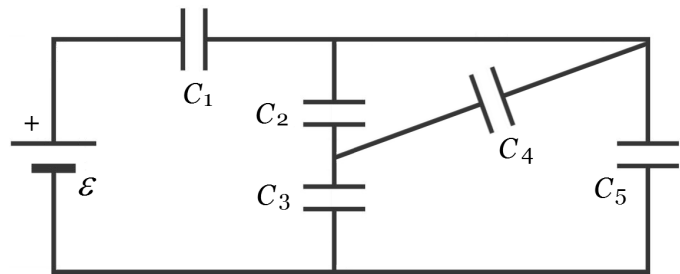Problem

In the circuit shown, which is subtly different from the circuit in the example, $C_1 = C_4 = C_5 = C$ and $C_2 = C_3 = 2C$.

- Find the equivalent capacitance of the circuit.
- Find the energy stored in capacitor C_4 . Express your answers in terms of C and \mathcal{E} .



- The only difference between this problem and the previous one is that capacitor C_4 is now in parallel with C_2 only. The equivalent capacitor C_{24} is then in series with C_3 .

$$C_{24} = C_2 + C_4 = 2C + C = 3C \quad \text{and} \quad C_{234} = \left[\frac{1}{C_{24}} + \frac{1}{C_3} \right]^{-1} = \left[\frac{1}{3C} + \frac{1}{2C} \right]^{-1} = \frac{6}{5}C$$

Those two are in parallel with C_5 .

$$C_{2345} = C_{234} + C_5 = \frac{6}{5}C + C = \frac{11}{5}C$$

Finally, capacitors C_1 and C_{2345} are in series, making the equivalent capacitance of the circuit:

$$C_{\text{eq}} = \left[\frac{1}{C_1} + \frac{1}{C_{2345}} \right]^{-1} = \left[\frac{1}{C} + \frac{5}{11C} \right]^{-1} = \frac{11}{16}C$$

- b) In order to find the energy stored in capacitor C_4 it is necessary to find the potential difference ΔV_4 across it. Starting with the equivalent capacitance, we can find the charge delivered by the battery.

$$Q_{\text{eq}} = C_{\text{eq}} \mathcal{E} = \frac{11}{16} C \mathcal{E}$$

Since C_1 and C_{2345} are in series, this is also the charge on each of them. The potential difference ΔV_{2345} can be found. Since C_{234} and C_5 are in parallel, this will be the potential difference across each of them.

$$\Delta V_{234} = \Delta V_{2345} = \frac{Q_{\text{eq}}}{C_{2345}} = \frac{11C\mathcal{E}/16}{11C/5} = \frac{5\mathcal{E}}{16}$$

The charge on C_{234} , then, is

$$Q_{234} = C_{234} \Delta V_{234} = \left(\frac{6C}{5} \right) \left(\frac{5\mathcal{E}}{16} \right) = \frac{3C\mathcal{E}}{8}$$

Since C_{24} and C_3 are in series, this is the charge on each of them. ΔV_{24} can then be found.

$$Q_{24} = Q_{234} \quad \text{so} \quad \Delta V_{24} = \frac{Q_{234}}{C_{24}} = \frac{3C\mathcal{E}/8}{3C} = \frac{\mathcal{E}}{8}$$

Since C_2 and C_4 are in parallel, this is also the potential difference across C_2 , so

$$U_4 = \frac{1}{2} C_4 (\Delta V_4)^2 = \frac{1}{2} C \left(\frac{\mathcal{E}}{8} \right)^2 = \frac{C\mathcal{E}^2}{128}$$